

**NED UNIVERSITY OF ENGINEERING & TECHNOLOGY, KARACHI**  
**FIRST YEAR (COMPUTER SCIENCE AND INFORMATION TECHNOLOGY)**

ANNUAL EXAMINATION 2007

BATCH 2006-07

Time: 3 Hours

Dated: 12-11-2007

Max. Marks: 80

**ELECTRICAL TECHNOLOGY**  
**FUNDAMENTALS – (EE-115)**

**Instructions:**

**1-Attempt any five questions,**

**2-All questions carry equal marks**

- Q1(a) Using the Voltage dividing Rule, determine voltages  $V_1, V_2$  and  $V_3$  for the series circuit of Fig #1. Hence prove that the circuit follows KVL Principle ie  $E = \sum V$  [08]
- Q1(b) A portion of a residential service to a network is shown in Fig # 2 [08]
- (i) Determine the current through each parallel branch of the network
- (ii) Calculate the current drawn from 120 V source. Will the 20A Circuit Breaker trip ?
- (iii) What is the total resistance of the network?
- (iv) Determine the Power supplied by 120 V source. How does it compare to the total power of the load?
- Q2(a) Define Thevenin's Theorem. Describe and apply the rules to find the Thevenin Equivalent circuit for Fig # 3. [08]
- Q2(b) Write the mesh equations for the circuit of Fig # 4. & Solve for the branch current through resistor  $R_3$ . [08]
- Q3(a) Apply Superposition Theorem to Fig # 5 to find current  $I_2$  through 12 K $\Omega$  resistor [08]
- Q3(b) Write the nodal equations for the circuit of fig # 6 & using determinants solve for the nodal voltages. [08]
- Q4(a) Define frequency response? Discuss the frequency response for the basic circuit elements R, L and C. [08]
- Q4(b) The voltage across a 1  $\mu$ F capacitor is given below. Write down the sinusoidal expression for the current? Also sketch the curve between  $v$  &  $i$ . [08]
- (i)  $v = 20\sin 400t$
- (ii)  $v = 30\sin(400t - 70^\circ)$ .
- Q5(a) Find the average value of the periodic waveforms shown in Fig # 7 [08]
- Q5(b) Discuss the Importance of Electrical Technology to the Modern World. [08]
- Q6(a) Using Voltage Dividing Rule, find the unknown voltages  $v_R$  and  $v_I$  for the circuit of Fig # 9 [07]
- Q6(b) For the network of Fig # 10 [09]
- (i) Find the Admittance of each parallel branch
- (ii) Determine the input Admittance
- (iii) Calculate the input Impedance
- (iv) Draw the Admittance Diagram
- Q7(a) Find the value of  $i$  required to establish flux of  $\phi = 0.75 \times 10^{-4}$  wb in the series magnetic circuit of Fig # 11 [08]



Q7(b) Discuss

- (i) Ferromagnetic Materials
- (ii) Permeability and Permittivity
- (iii) Air Gap
- (iv) Fringing Effect

[08]

Q8(a) Discuss the advantages and disadvantages of Permanent Magnet Moving Coil (PMMC) instruments.

[08]

Q8(b) What are Instrument Transformers ? Discuss.

[08]



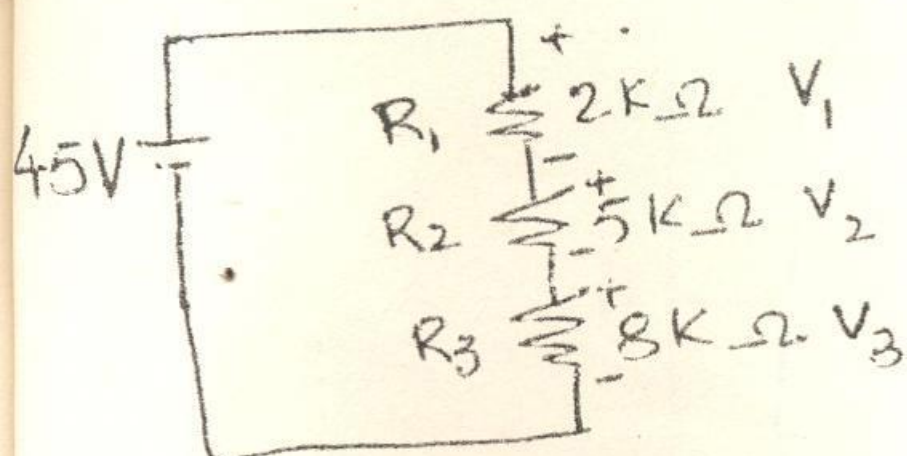


Fig # 1

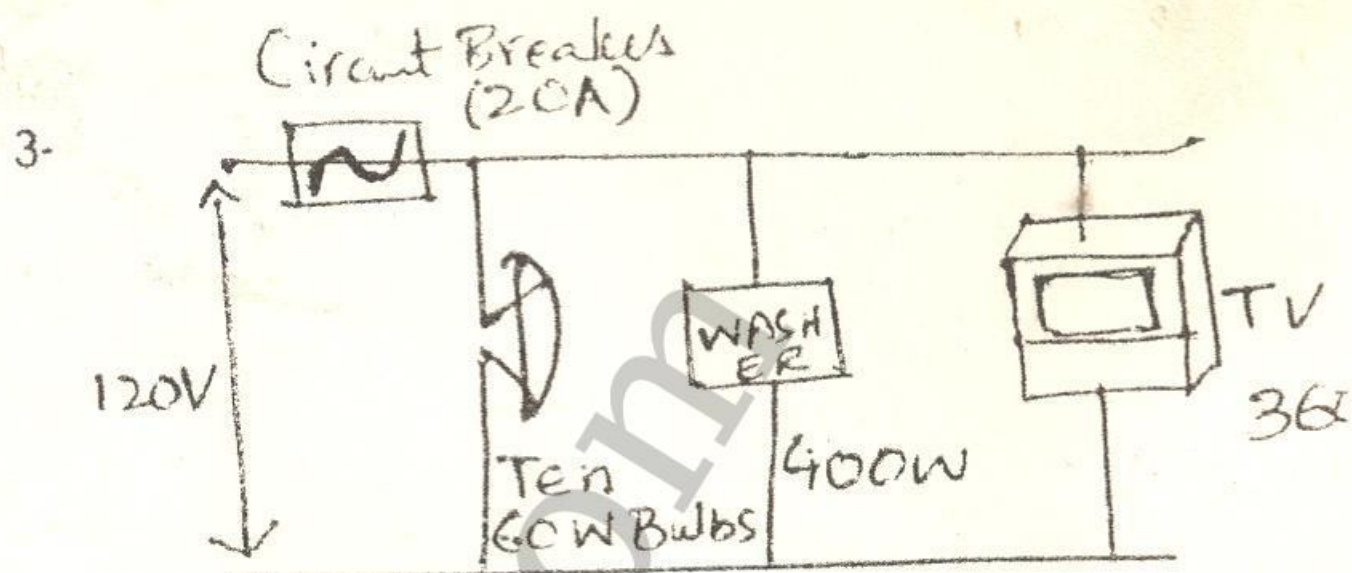


Fig # 2

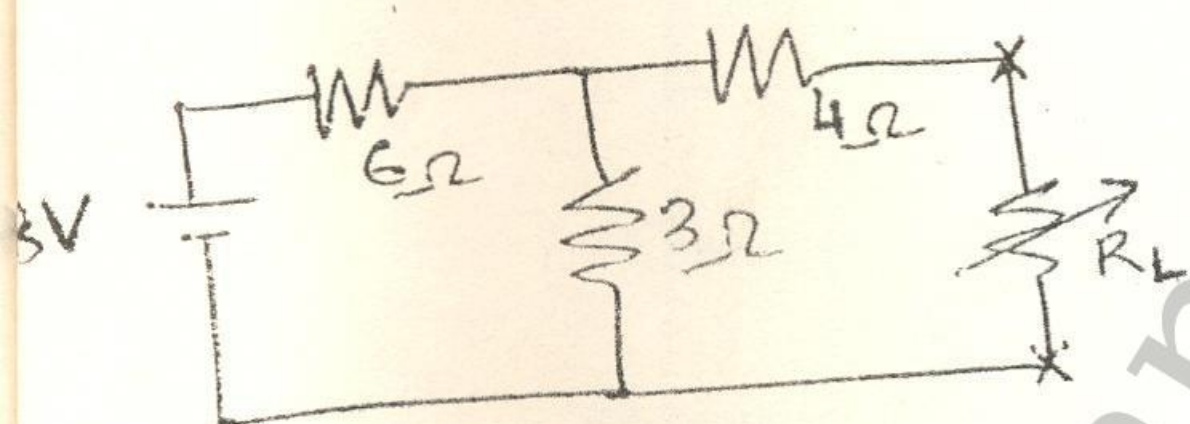


Fig # 3

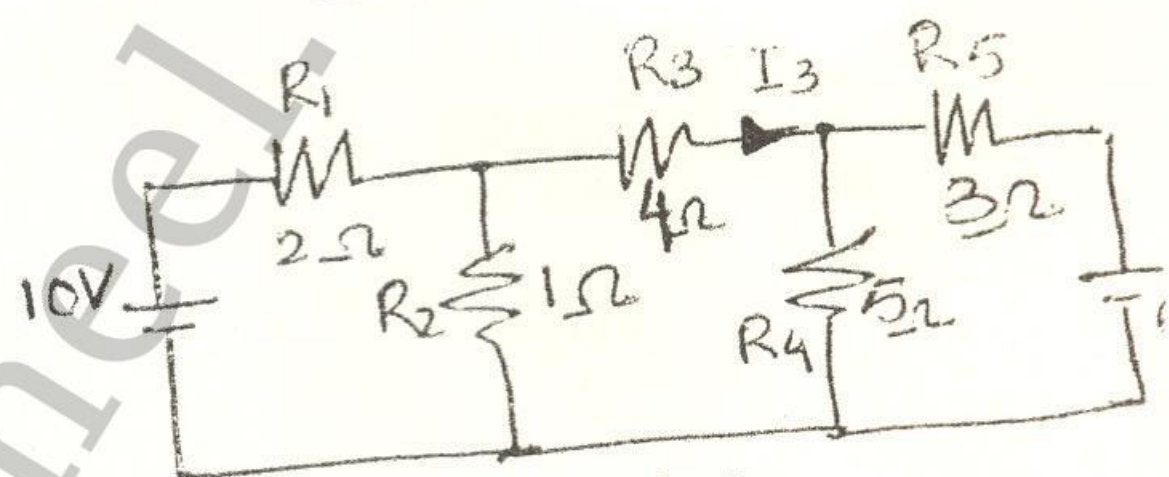


Fig # 4

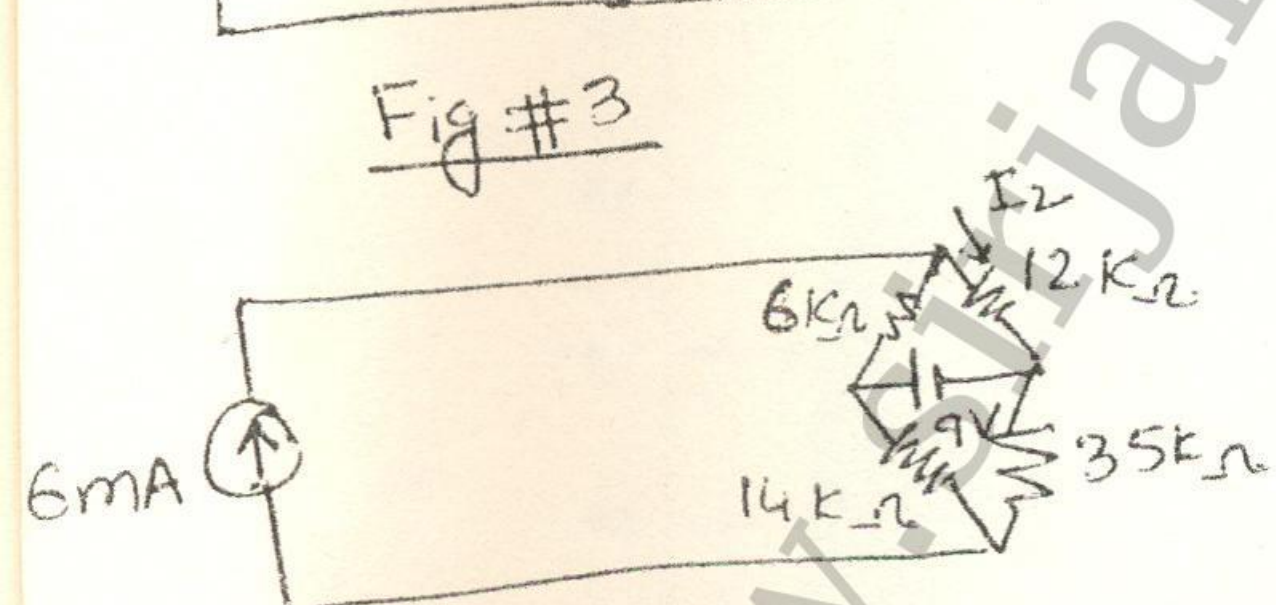


Fig # 5



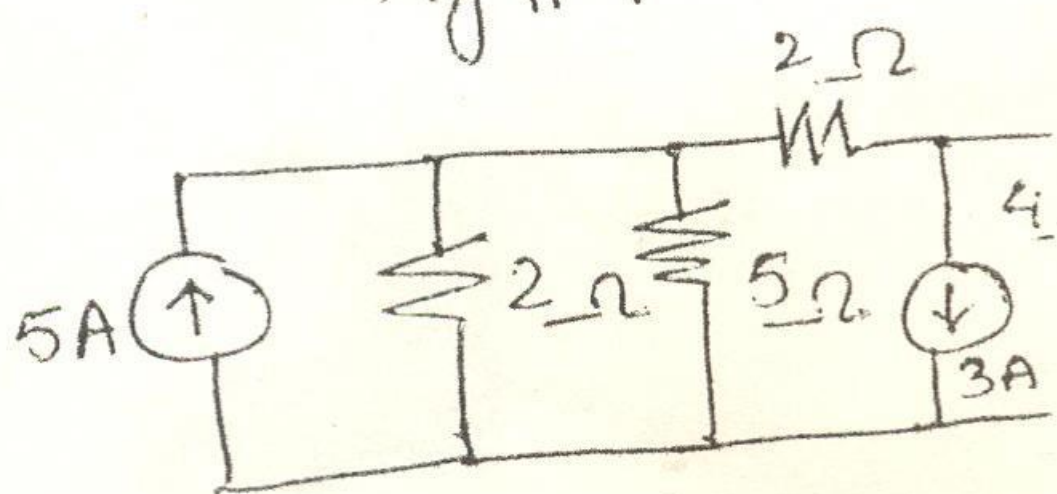


Fig # 6

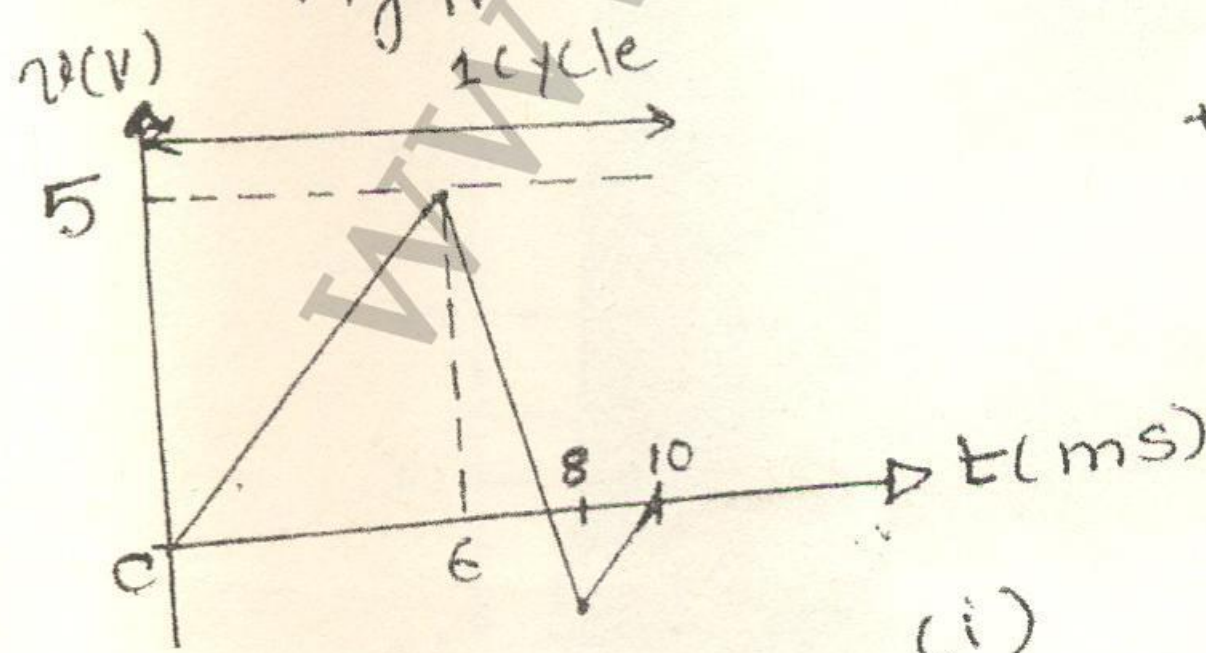

(i)

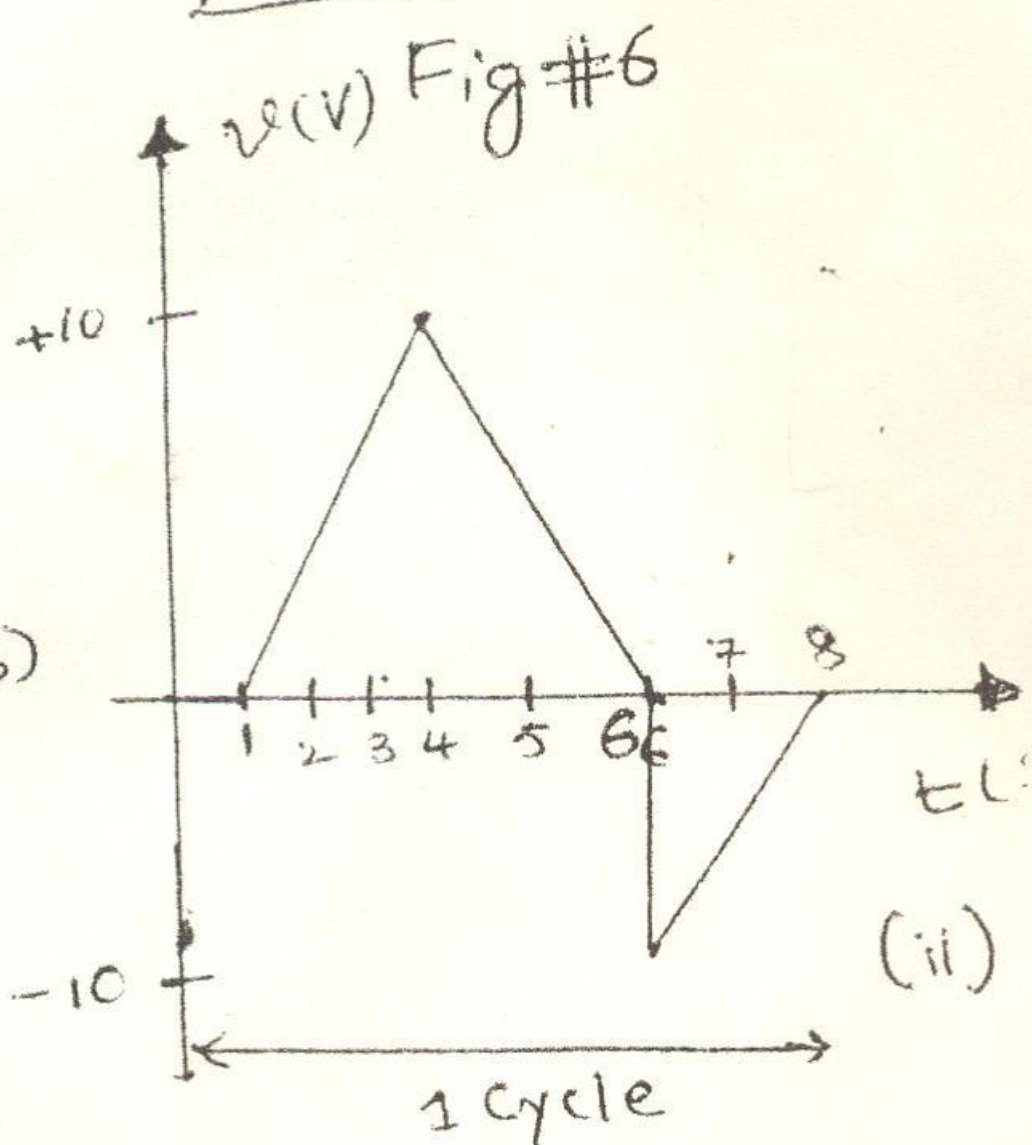

(ii)

Fig # 7



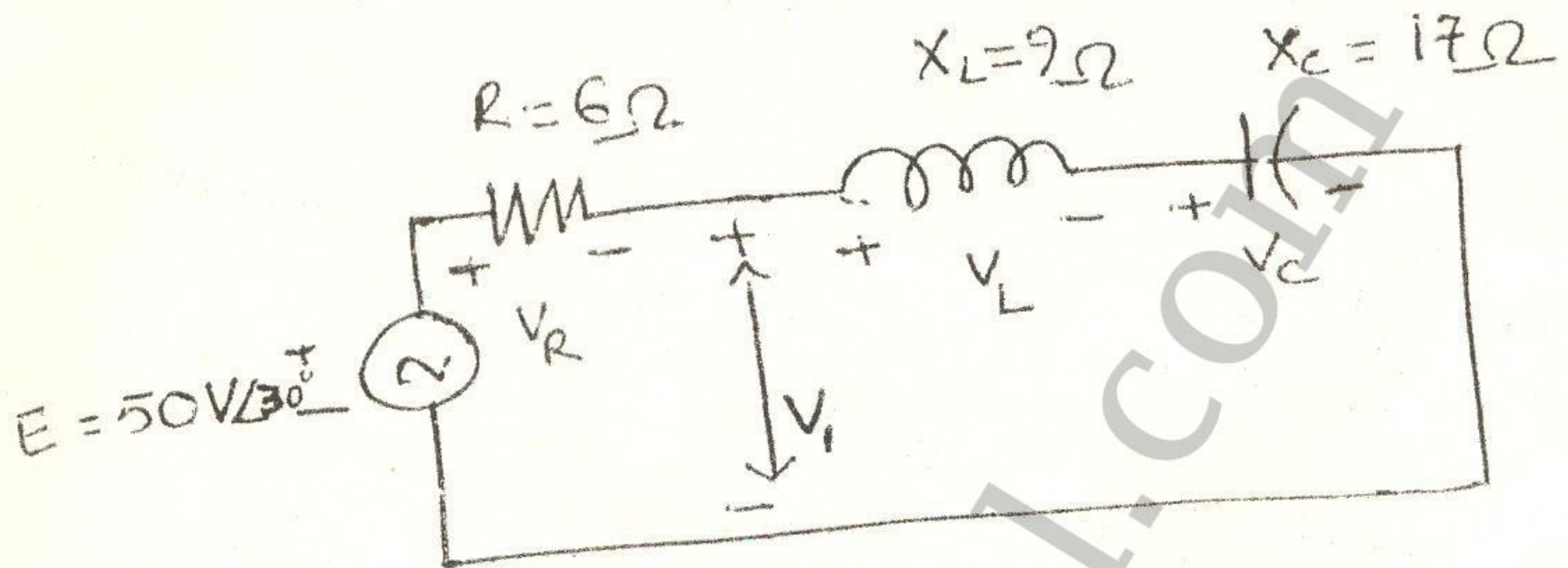


Fig # 9

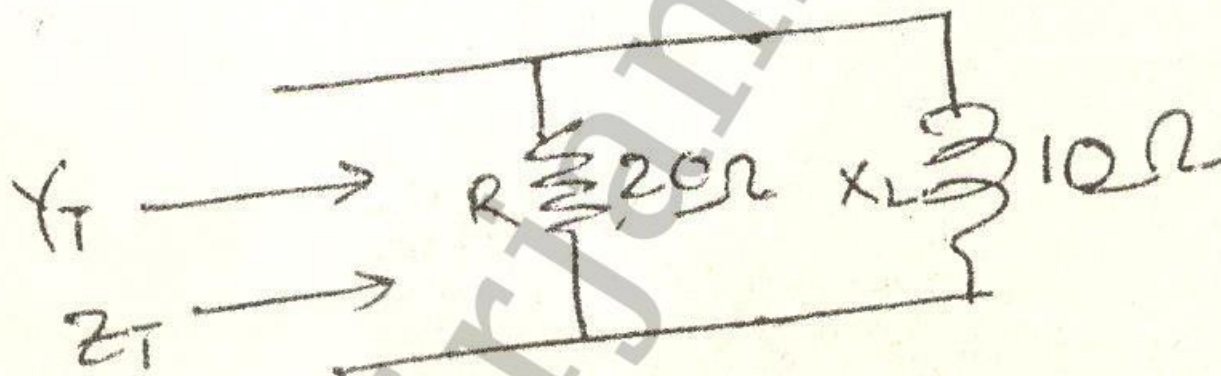


Fig # 10

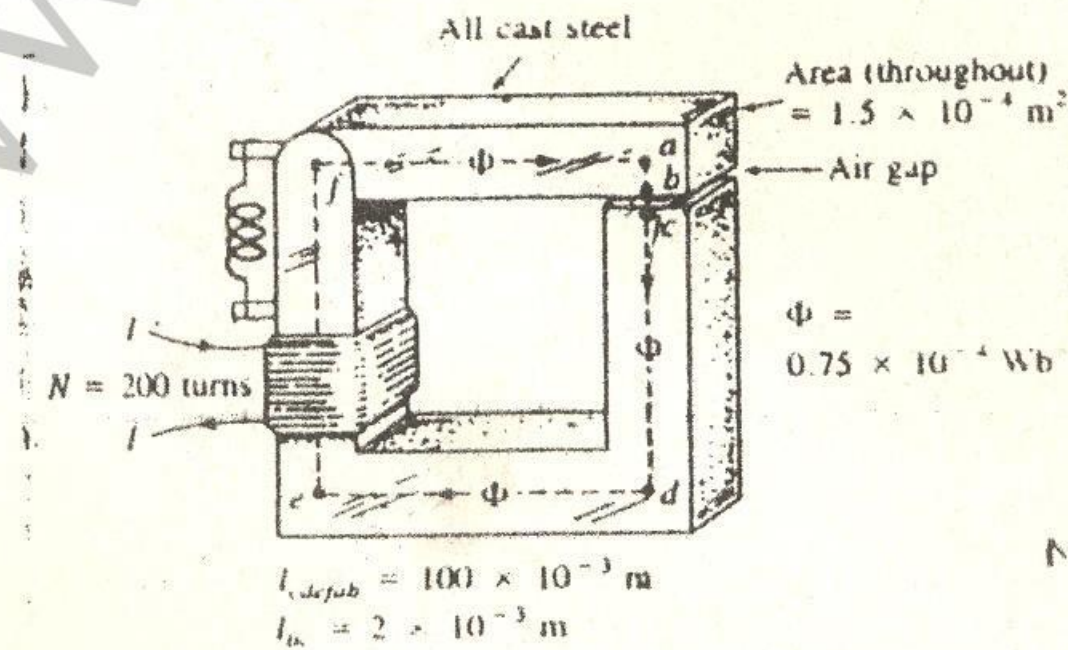


Fig # 11



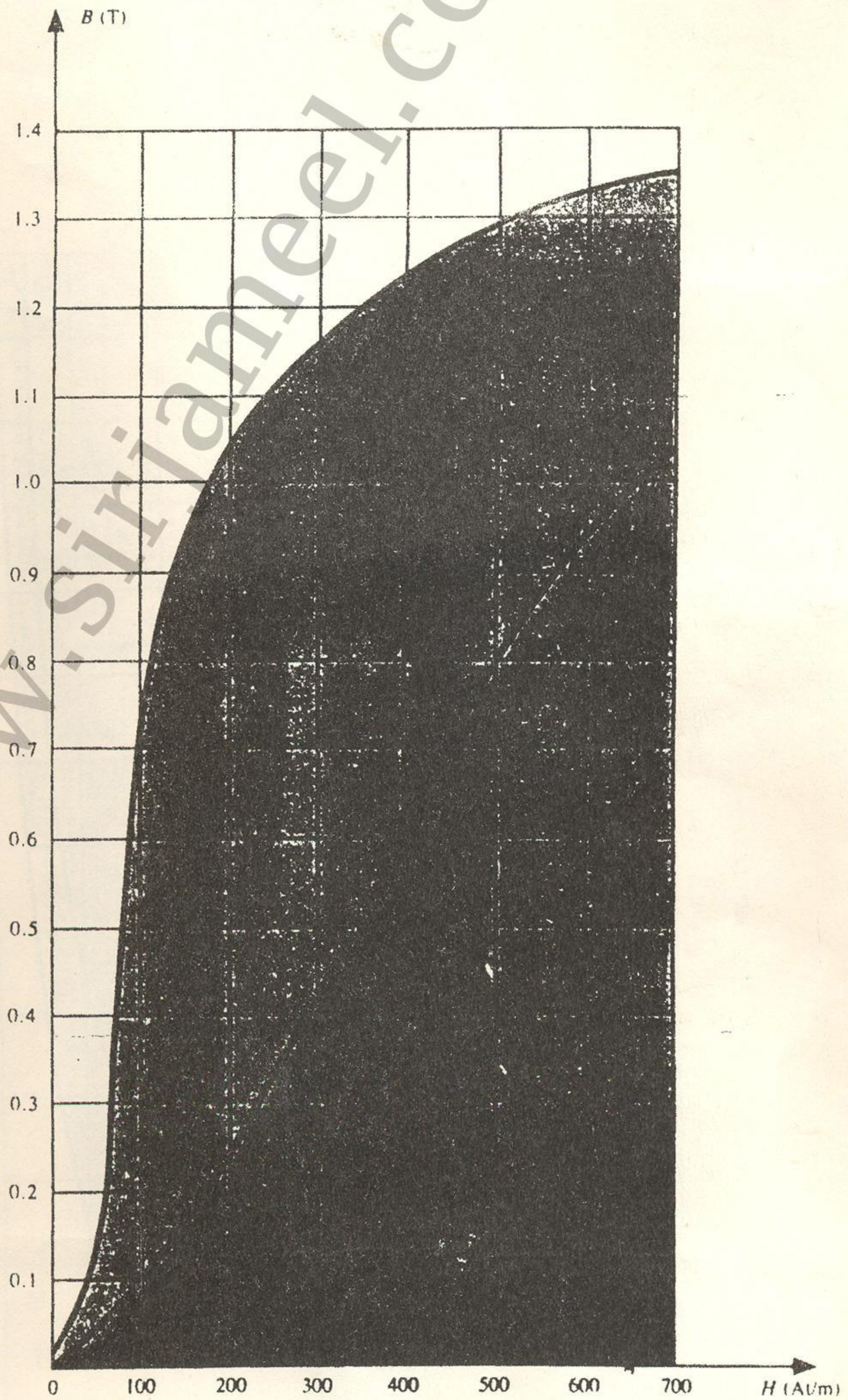


FIG. 11.22



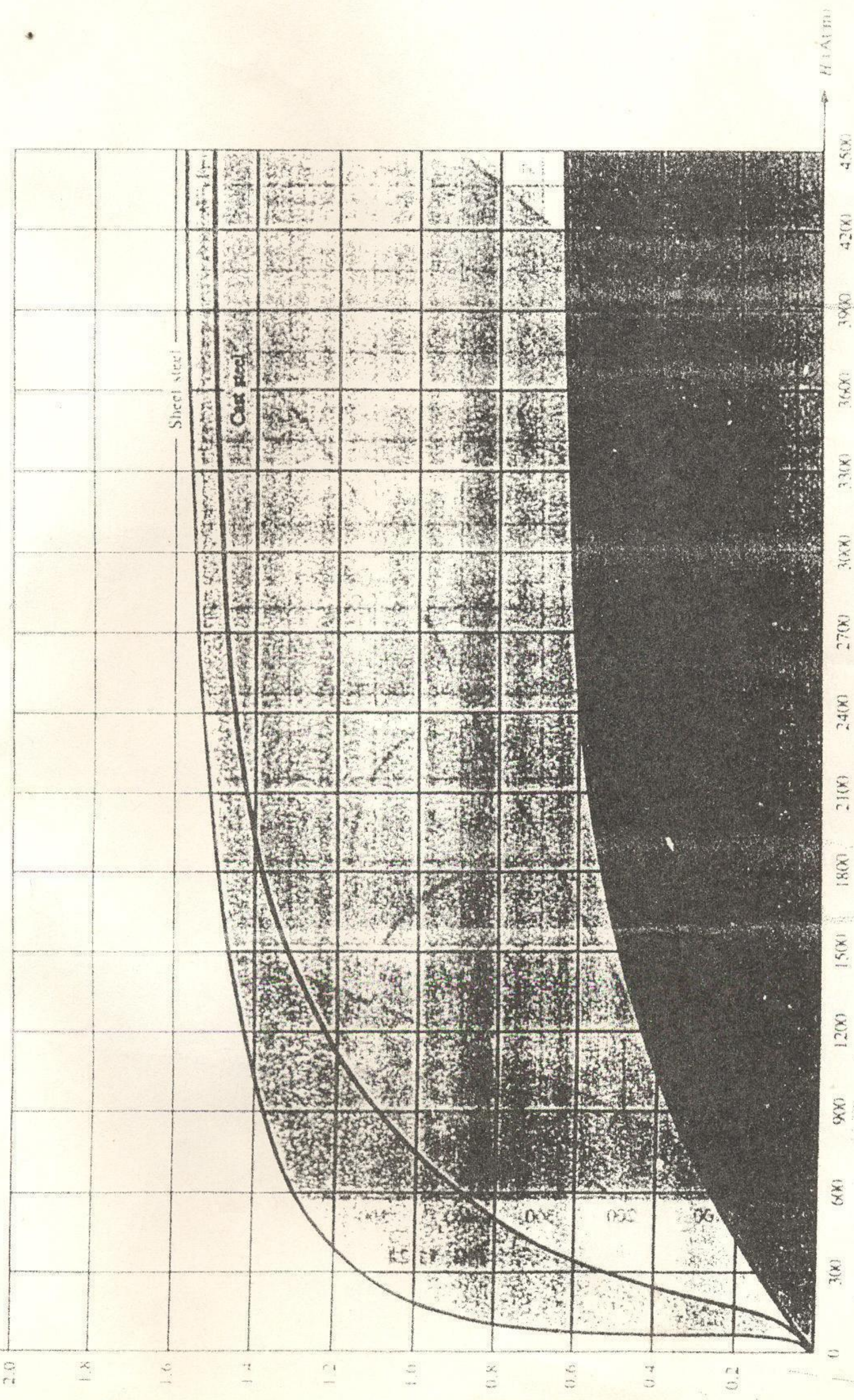


FIG. 11.21

www.sirjameel.com